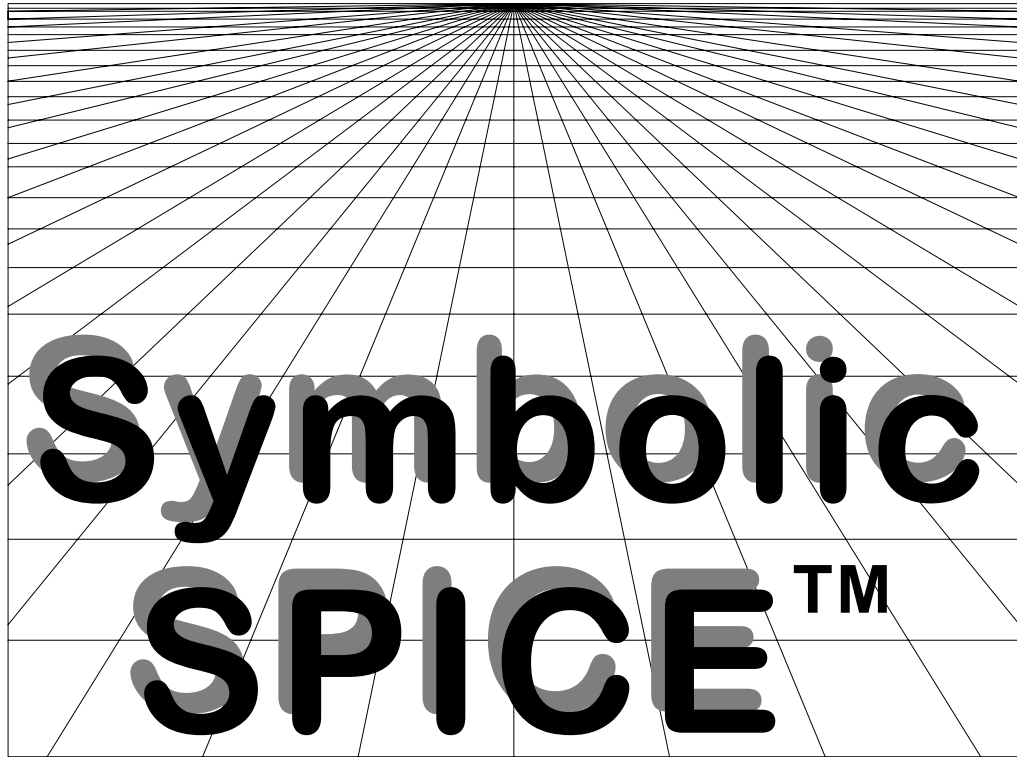


Symbolic SPICE



Circuit Analyzer and Approximator

## Application Note

AN-003:


Notch Filter Using a Simulated Inductor

by Gregory M. Wierzba

## A) Introduction

The schematic shown in Fig. 1 is a notch filter which uses a series resonant circuit [1-2]. At the resonant frequency [3] of  $1/(2\pi L_1 C_1)$ ,  $L_1$  and  $C_1$  form a short circuit. The resulting circuit is a differential amplifier with a difference of inputs equal to zero resulting in an output voltage of zero. Off resonance  $L_1$  and  $C_1$  act like an open circuit which forces  $V_1 = V_4 = V_3 = V_2$ . This produces a gain with a magnitude of one. Thus there is a notch at the frequency of  $f_o = 1/(2\pi L_1 C_1)$ .

A Symbolic SPICE™ input file, **notch.cir**, is given in Table 1. This file uses Symbolic SPICE's definition [4] of an ideal op-amp which begins with the letters XOA.

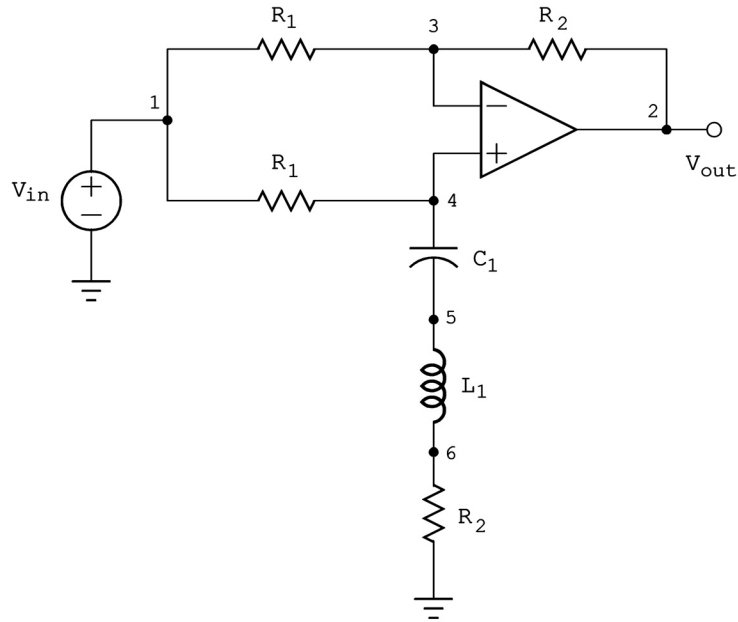

**Figure 1.** Notch filter

**Table 1.** Symbolic SPICE input file

```

Notch Filter
VS 1 0 AC 1
R1 1 3
R2 3 2
R1 1 4
R2 6 0
C1 4 5
L1 5 6
XOA 4 3 2
.END

```

## B) Running Symbolic SPICE

Running [4] the input file shown in Table 1, the following are the prompts. The user responses are shown in bold:

```
Symbolic SPICE - Circuit Analyzer and Approximator
Demo Version 3.1
(C) Copyright 2010 by Willow Electronics, Inc.

INPUT FILE NAME [.cir] : notch
OUTPUT FILENAME [notch.det] : (hit enter)
Determinant string sorted according to orders of some variable? (y/n) : n
Numerical evaluation of the results? (y/n) : n
Discard terms if their magnitude falls below a threshold? (y/n) : n
Check and solve for second order filter functions? (y/n) : y
FILTER FUNCTION FILE NAME [notch.fun] : (hit enter)
Solve for a variable or expression? (y/n) : y
Available Unknowns:
V1 V2 V3 V5 V6 V8
*Ignore nodes 7 and higher if present. They are used for internal numbering.
Valid Operators: +, -, *, /, ( ), { }, [ ]
Equation: v2
Solve for another variable or expression? (y/n) : n
```

## C) Symbolic SPICE Determinant Output

The output file **notch.det** listed in Table 2 is the matrix written by Symbolic SPICE and the transfer function requested.

**Table 2.** Symbolic SPICE Output File **notch.det**

```
Notch Filter

[0 ] [-G1      -G2      G2+G1      0      0      0      ] [V1 ]
[0 ] [-G1      0      sC1+G1     -sC1     0      0      ] [V2 ]
[0 ] = [0      0      -sC1      sC1-1    0      1      ] [V3 ]
[0 ] [0      0      0      -sL1     G2+1    sL1-1    ] [V5 ]
[1 ] [1      0      0      0      0      0      ] [V6 ]
[0 ] [0      0      0      sL1+1    -1     -sL1     ] [V8 ]

*Ignore nodes 7 and higher if present. They are used for internal numbering.

Numerator of: v2

TERMS SORTED ACCORDING TO POWERS OF s

s**2 terms:
```

```

+ sL1*sC1*G2*G1
s**0 terms:
+ G2*G1
*****
Denominator of: v2
TERMS SORTED ACCORDING TO POWERS OF s
s**2 terms:
+ sL1*sC1*G2*G1
s**1 terms:
+ sC1*G2 + sC1*G1
s**0 terms:
+ G2*G1
*****

```

## D) Symbolic SPICE Filter Function Output

Symbolic SPICE will examine any transfer function to determine if its denominator is second order in the Laplace operator  $s$ . If this is the case then it finds the parameters associated with the different filter functions. Symbolic SPICE finds formulas for  $Q_o$ ,  $\omega_o$  and  $H_i$  [4].

The output file **notch.fun** listed in Table 3 contains the filter parameters solved for by Symbolic SPICE.

**Table 3.** Symbolic SPICE Output File **notch.fun**

```

Notch Filter
SECOND ORDER FILTER PARAMETERS:
Qo is:
( + G1*G2)*SQRT{ + L1}
-----
( + G2 + G1)*SQRT{ + C1}
Wo**2 is:
( + 1)
-----
( + L1*C1)
*****

```

There exists a BAND STOP filter for : v2

BAND STOP GAIN (Hbs) is:

$$\frac{(+1)}{+1}$$

BAND STOP FREQUENCY (Wz\*\*2) is:

$$\frac{(+1)}{(+L1*C1)}$$

\*\*\*\*\*

Symbolic SPICE's format is a collection of strings of symbols. This is usually not how most people view equations, so you may need to do some minor editing. Thus we have:

$$Q_o = \frac{G_1 G_2}{G_2 + G_1} \sqrt{\frac{L_1}{C_1}} = \frac{1}{R_2 + R_1} \sqrt{\frac{L_1}{C_1}}$$

$$\omega_o = \omega_z = \frac{1}{\sqrt{L_1 C_1}}$$


The results show that the band-stop's frequency  $\omega_z$  is the same as the center frequency  $\omega_o$ . This implies that our band-stop filter is a notch filter. Also the gain off the notch frequency,  $H_{bs}$ , is one.

Another useful formula is that of the -3 dB bandwidth (radians/sec)

$$\text{Bandwidth} = \frac{\omega_o}{Q_o} = (R_2 + R_1) \sqrt{\frac{C_1}{L_1}} \frac{1}{\sqrt{L_1 C_1}} = \frac{(R_2 + R_1)}{L_1}$$

## E) Simulated Inductor

Most active filters avoid the use of inductors because of mutual inductance effects with the power supply transformer or other inductive circuit elements. Since there is a series resistor with the inductor of Fig. 1, we can use a lossy simulated inductor [1]. This is shown in Fig. 2. The Symbolic SPICE input file, **lossy\_L.cir**, is given in Table 4. *Note that when a current source of 1 A is used as an input then each node voltage is a transfer impedance and more specifically the input node voltage is the input impedance.*

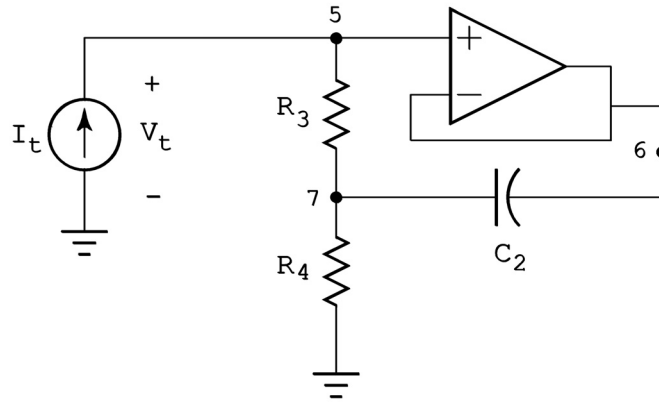

**Figure 2.** Lossy simulated inductor

**Table 4.** Symbolic SPICE input file **lossy\_L.cir**

```

SIMULATED INDUCTOR
It 0 5 AC 1
R3 5 7
R4 7 0
C2 6 7
XOA 5 6 6
.END

```

Running the input file shown in Table 4, the following are the prompts. The user responses are shown in bold:

```

Symbolic SPICE - Circuit Analyzer and Approximator
Demo Version 3.1
(C) Copyright 2010 by Willow Electronics, Inc.

```

```

INPUT FILE NAME [.cir] : lossy_L.cir
OUTPUT FILENAME [lossy_L.det] : (hit enter)
Determinant string sorted according to orders of some variable? (y/n) : n
Numerical evaluation of the results? (y/n) : n
Check and solve for second order filter functions? (y/n) : n
Solve for a variable or expression? (y/n) : y
Available Unknowns:
V5 V7
*Ignore nodes 8 and higher if present. They are used for internal numbering.
Valid Operators: +, -, *, /, (), {}, [ ]
Equation: v5
Solve for another variable or expression? (y/n) : n

```

## F) Symbolic SPICE Determinant Output

The output file `lossy_L.det` listed in Table 5 is the matrix written by Symbolic SPICE and the transfer function requested.

**Table 5.** Symbolic SPICE Output File `lossy_L.det`

```

SIMULATED INDUCTOR

[1 ]=[G3                               -G3                               ] [V5 ]
[0 ] [-sC2-G3                          sC2+G4+G3                          ] [V7 ]

*Ignore nodes 8 and higher if present. They are used for internal numbering.

Numerator of: v5

TERMS SORTED ACCORDING TO POWERS OF s

s**1 terms:

+ sC2

s**0 terms:

+ G4 + G3

*****

Denominator of: v5

TERMS SORTED ACCORDING TO POWERS OF s

s**0 terms:

+ G4*G3

*****

```

After some minor editing, we have

$$Z_{in} = \frac{V_t}{I_t} = \frac{V_5}{1} = \frac{sC_2 + G_4 + G_3}{G_4G_3} = s \frac{C_2}{G_4G_3} + \frac{G_4 + G_3}{G_4G_3} = sC_2R_4R_3 + (R_4 + R_3)$$

For our simulated inductor to work in Fig. 1, we want


$$Z_{in} = sL_1 + R_2$$

Thus we have

$$L_1 = C_2R_4R_3 \quad \text{and} \quad R_2 = (R_4 + R_3)$$

## G) Notch Filter Design

Putting together Figs. 1 and 2, we have the following filter:

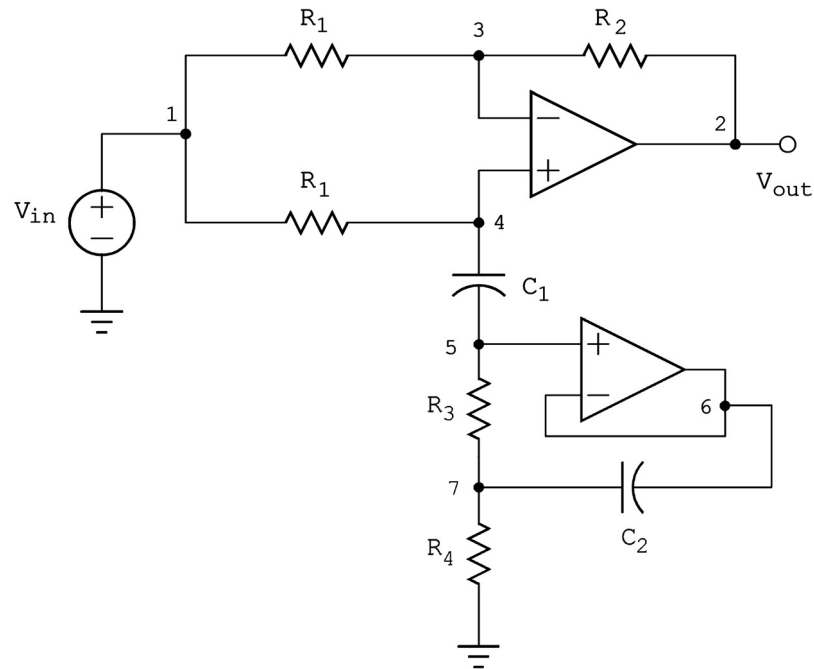

**Figure 3.** Notch filter using a simulated inductor

We can develop a design procedure using our formulas[1]:

- 1) Pick  $R_3 = R_4 = R$  to be a standard value
- 2) Let  $R_1 = R_2 = 2 R$
- 3)  $L_1 = (R_2 + R_1)Q_o / \omega_o = C_2 R_4 R_3$  then  
 $C_2 = (R_2 + R_1)Q_o / (R_4 R_3 \omega_o) = 4 Q_o / (R \omega_o)$
- 4)  $C_1 = 1 / (L_1 \omega_o^2) = 1 / (C_2 R^2 \omega_o^2)$


Suppose we design a notch for  $f_o = 120$  Hz with a  $Q_o$  of 5 then

- 1) Pick  $R_3 = R_4 = R = 10\text{k } \Omega$
- 2) Let  $R_1 = R_2 = 2 R = 20\text{k } \Omega$
- 3)  $C_2 = 4 Q_o / (R \omega_o) = 4 \cdot 5 / (10\text{k} \cdot 2\pi \cdot 120) = 2.6526\mu \text{ F}$
- 4)  $C_1 = 1 / (C_2 R^2 \omega_o^2) = 1 / [(2.6526\mu (10\text{k} \cdot 2\pi \cdot 120)^2] = 6631\text{p F}$

Let's verify the design with PSpice.

**Table 6.** PSpice input file for notch filter

```
Notch Filter
VIN 1 0 AC 1
R1 1 3 20K
R2 3 2 20K
R5 1 4 20K
R3 5 7 10K
R4 7 0 10K
C1 4 5 6631P
C2 6 7 2.6526U
X1 4 3 2 OPAMP
X2 5 6 6 OPAMP
.SUBCKT OPAMP 1 2 3
RI 1 2 100MEG
EA 3 0 1 2 100MEG
.ENDS OPAMP
.AC OCT 1000 60 240
.PROBE
.END
```

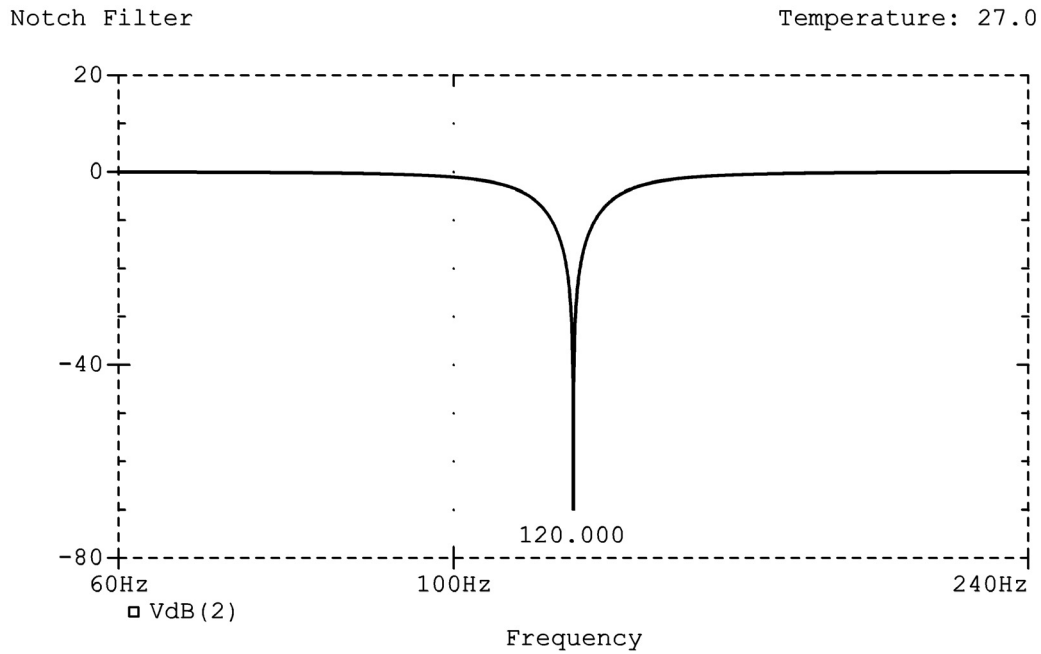

**Figure 4.** Magnitude of the voltage gain versus frequency

## H) Conclusion

Symbolic SPICE can be used to analyze ideal op-amp circuits to find transfer functions and input impedance. Symbolic SPICE can recognize second order transfer functions in the Laplace operator  $s$ . It can also determine the filter type such as band-stop and then solve for the filter parameters  $Q_o$ ,  $\omega_o$  and  $H_{bs}$ .

## I) References

- [1] D. Stout and M. Kaufman, "*Handbook of Operational Amplifier Circuit Design*," McGraw-Hill, pp. 13.1-13.4, 1976.
- [2] G. M. Wierzba, *ECE 402: Application of Analog ICs Class Notes*, Ch.2 , pp. 54-57. This e-book is available at <http://stores.lulu.com/willowepublishing>
- [3] G. M. Wierzba, *AN-001: Series Resonant Circuit*. This application note is available at [www.willowelectronics.com](http://www.willowelectronics.com)
- [4] G. M. Wierzba, *Symbolic SPICE User Manual*. This e-book is available at <http://stores.lulu.com/willowepublishing>